



**ELIZADE UNIVERSITY**  
**ILARA-MOKIN**  
**ONDO STATE**

**FACULTY: Basic and Applied Sciences**  
**DEPARTMENT: Physical and Chemical Sciences**  
**SECOND SEMESTER EXAMINATIONS**  
**2018/2019 ACADEMIC SESSION**

**COURSE CODE: PHY 208**

**COURSE TITLE: WORK SHOP PRACTICE I**

**DURATION: 3 HOURS**

**HOD's SIGNATURE**

**TOTAL MARKS:**

**Matriculation Number:** \_\_\_\_\_


**INSTRUCTIONS:**

1. Write your matriculation number in the space provided above and also on the cover page of the exam booklet.
2. This question paper consists of 2 pages with printing on both sides.
3. Answer all questions in the examination booklet provided.

**GIVEN COMPONENTS:** IC LM35, IC LM741, Resistors, Preset, LED (Red and Green), 9V Battery/ power supply, wire

**THEORY:** The IC741 is a non-inverting amplifier which means pin-3 is the input and the output is not inverted. The LM35 circuit has two input terminals namely; non-inverting (+) and inverting (-) terminals and only one output pin. This sensor circuit amplifies the difference between its input terminals. The advantages of this circuit are as follow; no effect on the medium, more accurate, it has an easily conditioned output and it responds instantly.

**CIRCUIT:**

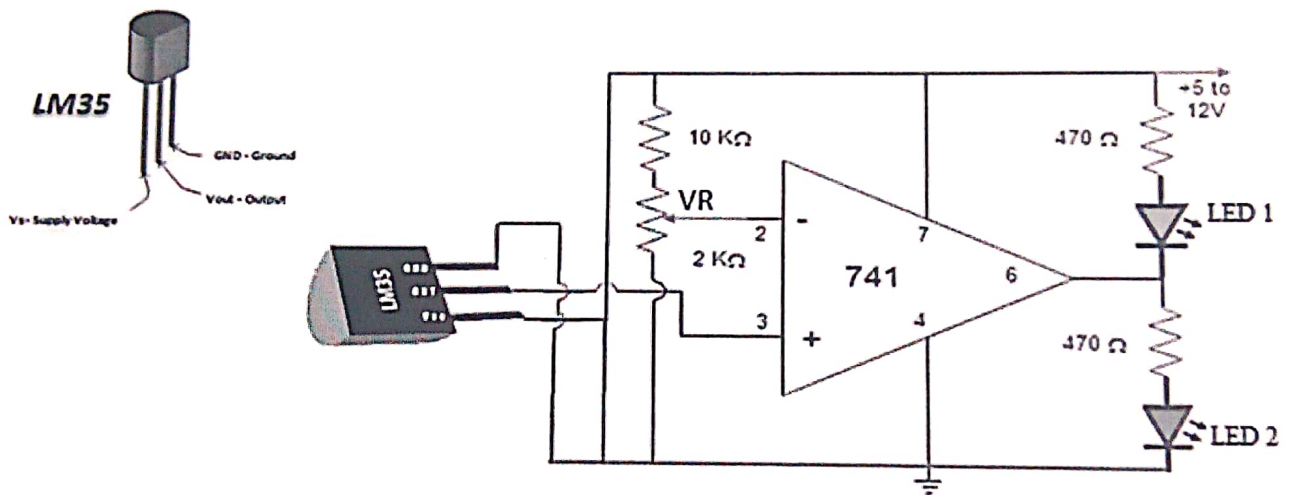

1. What type of IC is LM35 and LM741?
2. Draw the circuit lay out of the above circuit diagram
3. State the function of the following in the circuit above
  - (i) Variable Resistor VR
  - (ii) LM317
  - (iii). LM741
4. Suggest a title for this circuit diagram with the reason and state one major advantage of it
5. State three other applications of LM35
6. When does LED 1 and 2 light up