



ELIZADE UNIVERSITY, ILARA-MOKIN, ONDO STATE
FACULTY OF ENGINEERING
DEPARTMENT OF ELECTRICAL AND COMPUTER ENGINEERING

SEMESTER II EXAMINATION, 2015/2016 ACADEMIC SESSION

COURSE TITLE: ELECTRONIC CIRCUITS II

COURSE CODE: EEE 322

EXAMINATION DATE: 14TH JULY, 2016

COURSE LECTURER: DR AFARA, I.O.

A handwritten signature in black ink, enclosed in a rectangular box.

HOD's SIGNATURE

TIME ALLOWED: 2HRS

INSTRUCTIONS:

1. ANSWER QUESTION 1, AND ANY OTHER 2 QUESTIONS (TOTAL OF 3 QUESTIONS)
2. SEVERE PENALTIES APPLY FOR MISCONDUCT, CHEATING, POSSESSION OF UNAUTHORIZED MATERIALS DURING EXAM.
3. YOU ARE ALLOWED TO COME INTO THE EXAMINATION WITH A SINGLE A4 SHEET OF FORMULA (PRINTED AND NOT HANDWRITTEN). YOU ARE NOT ALLOWED TO SHARE OR DISTRIBUTE FORMULA SHEETS.
4. YOU ARE NOT ALLOWED TO BORROW CALCULATORS AND ANY OTHER WRITING MATERIALS DURING THE EXAMINATION.

QUESTION 1 (COMPULSORY): [40%]

(a). Convert the following codes:

i. 321_{10} to BCD_{8421}

ii. 001101110110 BCD_{8421} to decimal.

iii. 0001100101100110 BCD_{8421} to decimal.

(b). Evaluate the following:

i. $01010110 - 00100011$

ii. 0111×0101

iii. $01111000 / 110$

(c). List the different classes of binary codes and give examples of two.

(d). i. Explain how the two types of binary compliments can be obtained.

ii. Evaluate $0011010 - 001100$ using the binary compliments method.

QUESTION 2: [30%]

(a). Prove the De Morgan's theorem by *perfect induction* (show the truth table).

(b). Simplify the logic expressions U and V using Boolean algebra:

i. $U = (AB(C + \overline{BD}) + \overline{AB})CD + ABCD$

ii. $V = \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + A\overline{B}\overline{C} + A\overline{B}C$

(c). Given the following logic expressions:

$$f = \overline{A}B\overline{D} + BCD + \overline{A}B\overline{C}D + CD$$

$$g = (\overline{A} + \overline{B} + C + D)(\overline{A} + B + \overline{C} + \overline{D})(A + B + \overline{C} + D)(\overline{A} + \overline{B} + \overline{C} + \overline{D}) \\ (A + B + \overline{C} + \overline{D})$$

i. Express f and g in standard form (if necessary),

ii. Minimize the expressions f and g using K-map,

iii. Implement the minimized expressions using AND and OR gates.

(d). Given the following populated Karnaugh maps:

		<i>CD</i>			
<i>AB</i>		00	01	11	10
00		1			1
01		1	1		1
11		1	1		1
10		1		1	1

(A)

		<i>CD</i>			
<i>AB</i>		00	01	11	10
00				0	0
01				0	
11		0	0	0	0
10				0	

(B)

- i. Simplify the logic expression represented on the maps,
- ii. Implement the minimized expressions using the basic logic gates.

QUESTION 3: [30%]

(a). What are combinational circuits, mention 3 of their characteristics, and list 6 examples of combinational circuits.

(b). Given the truth table of a full adder (Table 1):

- i. Obtain the expression for the carry bit C_o using K-map,
- ii. Synthesis the logic circuit for the expression using basic logic gates.

Inputs			Output	
A	B	C_{in}	S	C_o
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Table 1: Truth table of a full adder

(c). i. What are decoders and what are their functions? Give examples of decoders.

ii. Given the truth table of a special decoder (Table 2), obtain expressions for the outputs, and synthesis the logic circuit for the expressions using basic logic gates.

Inputs		Output			
A	B	D ₀	D ₁	D ₂	D ₃
0	0	1	0	0	0
0	1	0	1	0	0
0	1	0	0	1	0
1	1	0	0	0	1

Table 2: Truth table of a special decoder

QUESTION 4: [30%]

(a). What are sequential circuits? Mention 3 of their characteristics, and list 2 examples of sequential circuits.

(b). Differentiate, with the aid of diagrams, between synchronous and asynchronous sequential circuits.

(c). What are multivibrators and what are their functions?

(d). Mention the 3 common types of multivibrators and describe their main characteristics and operation in detail.