



ELIZADE UNIVERSITY ILARA MOKIN, ONDO
STATE

FACULTY OF ENGINEERING

DEPARTMENT OF ELECTRICAL AND
COMPUTER ENGINEERING

SECOND SEMESTER EXAMINATION, 2017/2018 ACADEMIC SESSION

COURSE TITLE: ELECTRONIC CIRCUIT II

COURSE CODE: EEE 322

EXAMINATION DATE: 1ST AUGUST 2018

COURSE LECTURER: DR K. O. TEMIKOTAN

A rectangular box containing a handwritten signature in black ink.

HOD's Signature

TIME ALLOWED: 2 HOURS 30 MINUTES

INSTRUCTION

1. ANSWER ALL QUESTIONS IN SECTION A AND FOUR QUESTIONS IN SECTION B
2. SEVERE PENALTIES APPLY FOR MISCONDUCT, CHEATING, POSSESSION OF UNAUTHORIZED MATERIALS DURING EXAM.
3. YOU ARE NOT ALLOWED TO BORROW ANY WRITING MATERIALS DURING THE EXAMINATION.

SECTION A

ANSWER ALL QUESTIONS IN THIS SECTION

- i. When is a 4-bit sum invalid in a BCD addition?

- ii. Convert 11011 in Gray to binary.

- iii. Which of these is not an alphanumeric code? (ASCII, Unicode, BCD, EBCDIC)
- iv. A NOT gate has $V_{IL} = 0.8\text{ V}$, $V_{IH} = 2.5\text{ V}$, $V_{OL} = 0.4\text{ V}$, and $V_{OH} = 3.6\text{ V}$. If two such gates are cascaded, find the high and low margins. Low noise margin is _____ and high noise margin is _____.
- v. In a sum of product logic circuit, the output gate is an _____ gate, while in a product of sum logic circuit, the output gate is an _____ gate.
- vi. The term fan-in means


_____ (2 Marks)
- vii. How many flip flops are required to divide a frequency by 32? _____
- viii. A counter has n flip flops, the number of states for the flip flop will be less or equal to _____.
- ix. Asynchronous counters are also called _____ counters
- x. A _____ is a circuit used to select and route any one of several input signals to a single output.
- xi. The main disadvantage of MOS ICs is _____ in comparison with TTL ICs.
- xii. If the output of a 2-input gate is defined by $Y = \bar{A}B + A\bar{B}$, the gate is a _____ gate
- xiii. What is the next number in the series 0 01 10 11 100 101 _____?
- xiv. Any logical circuit can be realized using either _____ gate or _____ gate.
- xv. Two functions of a shift register are _____ and _____ (20 Marks)

SECTION B

ANSWER ANY FOUR QUESTIONS

QUESTION ONE

 - a. The input waveforms applied to a 3-input AND gate are as indicated in Figure 1. Show the output waveform represented by X in proper relation to the inputs with a timing diagram.



(2 Marks)

Figure 1 Timing Diagram and Logic Symbol for Question 1

- b. Implement $Y = AB + C\bar{D}$ using only NAND gates (3 Marks)
 c. Design a logic circuit for decimal to BCD encoder. (5 Marks)

QUESTION TWO

- a. Using Karnaugh map minimize the expression;
 $Z = \bar{A}\bar{B}\bar{C} + A\bar{C}\bar{D} + A\bar{B} + ABC\bar{D} + \bar{A}\bar{B}C$ (4 Marks)

- b. Design the simplest circuit that has four inputs, A, B, C, and D, which produces an output value of 1 whenever three or more of the input variables have the value of 1; otherwise the output has to be 0. (6 marks)

QUESTION THREE

- a. Using a diode transistor logic (DTL) design a circuit that can implement;
 $X = \overline{(A + \bar{B} + C)}$ (4 marks)
 b. Draw the Truth Table for the circuit in Figure 2 and derive an expression for F (6 marks)

 


Figure 2 Logic Diagram for Question 3

QUESTION FOUR

- a. The min-term of a Boolean expression is given as;
 $Y = (A, B, C) = \sum m(1,3,5,6)$.

Implement this using a multiplexer.

(3 Marks)

- b. Write out the expression for Y and implement using discrete gates. (3 Marks)
- c. What is a demultiplexer? Given the following truth table for a DEMUX, identify the type and draw the logic circuit for the DEMUX. (4 Marks)

Table for Question 3c

A	B	D	A_0	A_1	A_2	A_3
0	0	0	0	0	0	0
0	0	1	1	0	0	0
0	1	0	0	0	0	0
0	1	1	0	1	0	0
1	0	0	0	0	0	0
1	0	1	0	0	1	0
1	1	0	0	0	0	0
1	1	1	0	0	0	1

QUESTION FIVE

- a. List and explain briefly five performance characteristics of an analogue to digital converter. 4 marks
- b. Draw a 4-bit R/2R ladder DAC and explain its principles of operation. (4 Marks)
- c. Determine the percentage resolution of the the following digital to analogue converters.
- An 8-bit DAC
 - A 16- bit DAC
- (2 Marks)

QUESTION SIX

- a. Show how a J K flip flop can be converted to a D flip flop. (2 Marks)
- b. A counter is required to count the number of bottles being automatically filled in a plant. Each time a bottle crosses an electronic sensor a pulse is generated. If 1000 bottles are to be counted, what is the minimum number of flip flops required? (2 marks)
- c. Determine the output of the DAC in Figure 3 if the input signal is 1011. D_0 is the least significant bit. Assume that binary 1 represents 5 V. (6 Marks)

 


Figure 3. DAC for Question 6c

(6 Marks)