



ELIZADE UNIVERSITY, ILARA-MOKIN, ONDO STATE
FACULTY OF ENGINEERING
DEPARTMENT OF ELECTRICAL AND COMPUTER ENGINEERING

SEMESTER I EXAMINATION, 2016/2017 ACADEMIC SESSION

COURSE TITLE: ELECTRIC CIRCUIT THEORY

COURSE CODE: EEE 317

EXAMINATION DATE: 4TH APRIL, 2017

COURSE LECTURER: DR R. O. Alli-Oke

A rectangular box containing a handwritten signature in black ink.

HOD's SIGNATURE

TIME ALLOWED: 2½ HRS

INSTRUCTIONS:

1. ANSWER QUESTION 1 AND ANY OTHER TWO QUESTIONS (TOTAL OF 3 QUESTIONS)
2. SEVERE PENALTIES APPLY FOR MISCONDUCT, CHEATING, POSSESSION OF UNAUTHORIZED MATERIALS DURING EXAM.
3. YOU ARE NOT ALLOWED TO BORROW CALCULATORS AND ANY OTHER WRITING MATERIALS DURING THE EXAMINATION.

1)

a)

- i) Differentiate between networks and circuits? (3 marks) Explain briefly what you understand by passive sign convention for circuit elements. (3 marks)
- ii) Determine the absorbed power by each of the circuit elements shown in the figure 1 below. (4 marks)

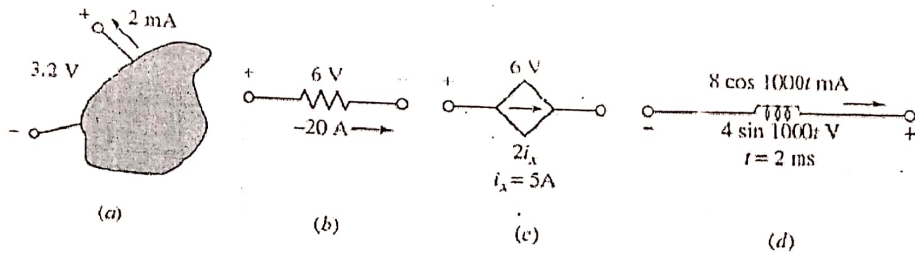


Figure 1: Circuit Elements

- b) Find the relation between V_1 and V_2 that must hold so that $I = 1A$. (3 marks)

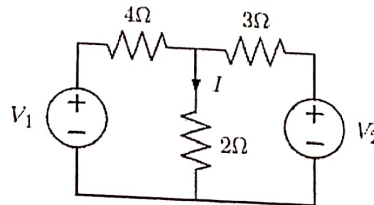


Figure 2: A 2-Loop Circuit

- c) The Parseval's theorem states that $\int_{-\infty}^{\infty} |x(t)|^2 dt = \frac{1}{2\pi} \int_{-\infty}^{\infty} |X(\omega)|^2 d\omega$ where $X(\omega) = F_{\omega}\{x(t)\} = \int_{-\infty}^{\infty} x(t) e^{-j\omega t} dt$ is the Fourier transform of the signal $x(t) = e^{-at}u(t)$ and find the bandwidth W such that 95% of the energy is contained in frequencies below W . (5 marks)
- d) Determine the steady-state current $i(t)$ shown in this circuit. Hint: use phasor-domain analysis (5 marks)

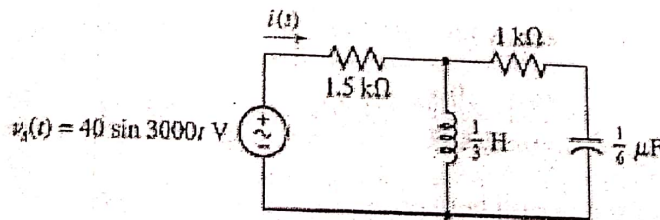


Figure 3: A Sinusoidal-Excited Circuit

- e) Design an analog passive band-pass filter that has a Q-factor of 0.8 and a bandwidth of 20 kHz. Use only resistors-capacitors combination for your design and assume that the center frequency is the midpoint of the bandwidth. (6 marks)

- c) A $5 \mu\text{F}$ capacitor with an initial voltage of 4V is connected to a parallel combination of a $3 \text{ k}\Omega$ and a $6 \text{ k}\Omega$ resistor. Find the current i in the $6 \text{ k}\Omega$ resistor. (5 marks).

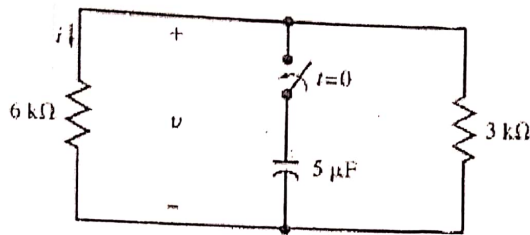


Figure 7: Source-Free RC Circuit

4)

- a) Differentiate between Laplace-Domain circuits and Phasor-Domain circuits (2 marks).
- b) Use phasor-domain analysis on the circuit shown in the figure (b) to determine the sinusoidal steady-state currents I_1 , and I_2 . (5 marks)

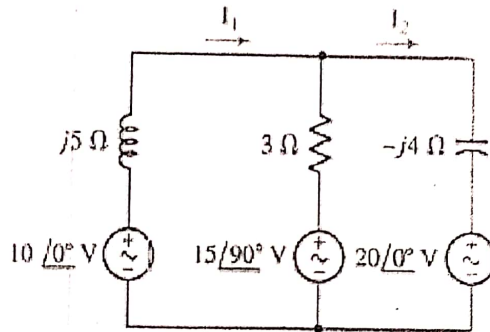


Figure 8: Phasor-Domain Analysis

- c) Consider the following circuit in figure 9. Assume the input is $V_i(t) = V_p \cos \omega t$.
- Use phasor-approach to determine $V_o(t)$ (3 marks)
 - Let V_i and V_o represents phasors corresponding to input and output voltages respectively. Determine the frequency transfer function $H(j\omega) = \frac{V_o}{V_i}$ (3 marks)
 - Classify the kind of filter is the R-C network is? Use at least 3 categories of classification. (3 marks)
 - Determine 3dB cut-off frequency analytically or otherwise (2 marks)

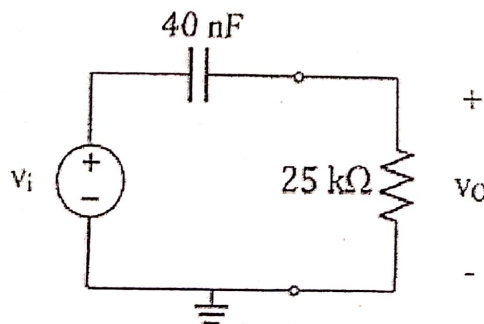


Figure 9: Filters - Phasor-Domain Analysis

2)

- a) State 3 electric circuit analysis techniques you know. (3 marks)
- b) Consider the following resistive circuit shown in figure 2.
- i) Determine the current through the 10Ω resistor (6 marks).
- ii) Compute the power absorbed by the 10Ω resistor (4 marks)

Hint: $\begin{bmatrix} -0.8 & 0.1 \\ 0.1 & -0.85 \end{bmatrix}^{-1} = \begin{bmatrix} -1.2687 & -0.1493 \\ -0.1493 & -1.1940 \end{bmatrix}$

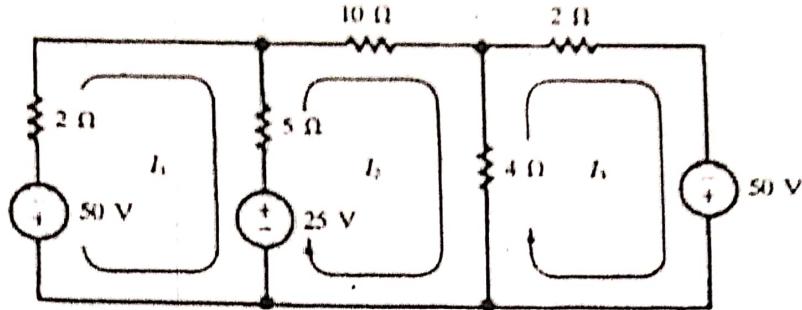


Figure 4: Resistive Circuit with DC sources.

- c) Using repeated source transformation, determine the Norton equivalent of network A. (5 marks)

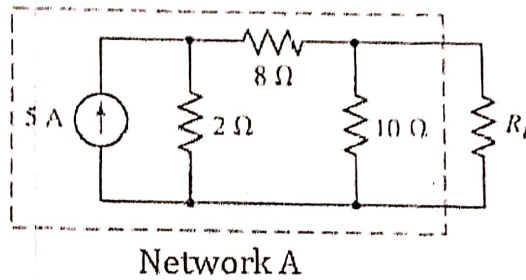


Figure 5: Source Transformation

3)

- a) Differentiate between Thevenin's theorem and Norton's theorem. (3 marks)
- b) Find the Thevenin's equivalent of the network shown in figure 6 as viewed from the following ports:
- i) port $x - x'$ (5 marks)
- ii) port $y - y'$ (5 marks)

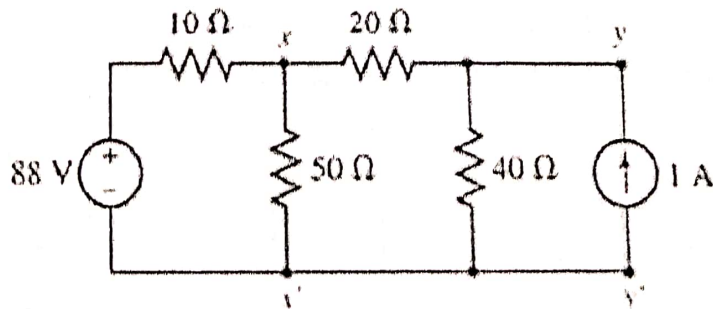


Figure 6: Multiple-Loop Circuit