



ELIZADE UNIVERSITY, ILARA-MOKIN, ONDO STATE  
FACULTY OF ENGINEERING  
DEPARTMENT OF ELECTRICAL AND COMPUTER ENGINEERING

SEMESTER II EXAMINATION, 2016/2017 ACADEMIC SESSION

COURSE TITLE: ELECTRONIC CIRCUIT II

COURSE CODE: EEE 322

EXAMINATION DATE: 26<sup>th</sup> JULY 2017

COURSE LECTURER: Dr. K. Temikotan

HOD's SIGNATURE

TIME ALLOWED: 2 hours 30 mins

**INSTRUCTIONS:**

1. ANSWER ANY FIVE QUESTIONS
2. SEVERE PENALTIES APPLY FOR MISCONDUCT, CHEATING, POSSESSION OF UNAUTHORIZED MATERIALS DURING EXAM.
3. YOU ARE **NOT** ALLOWED TO BORROW CALCULATORS AND ANY OTHER WRITING MATERIALS DURING THE EXAMINATION.
4. STATE CLEARLY THE COMBINED STOPPING CONDITIONS USED IN YOUR SOLUTIONS

**Question #1**

- a. Design the simplest circuit that implements the following function using only NAND gates

$$f(A, B, C) = \sum m(3,4,6,7) \quad (8 \text{ marks})$$

- b. In the diagram Fig Q1, the box represents a logical element which produces a TRUE output only when majority of the three inputs W, X, and Y are TRUE. Express Z as sum of products of the input variables. Draw an equivalent logical diagram for the box. (12 marks)

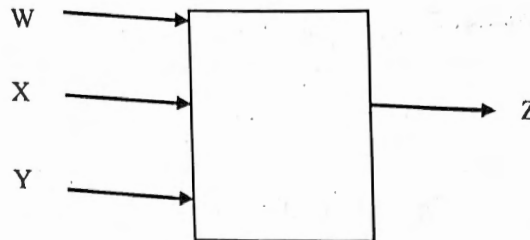


Fig Q1 for Question 1

**Question #2**

- a. The wave patterns show the inputs A and B and the output X from a basic logic gate. Identify the logic gate used and draw the truth table for the gate (6 marks)

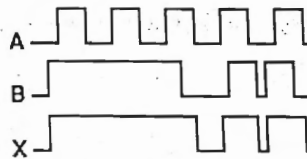


Fig Q2 for Question 2

- b. A chemical process requires that temperature T and pressure P be monitored so that an alarm sounds as and when either temperature or pressure exceeds reference values. Draw a block diagram of the system showing the logic to activate the alarm. Use a truth table to illustrate the condition of operation of the system. Clearly explain how the system operates. (14 marks)

**Question #3**

- a. Find the 2's complement of -20; and 26 (10 marks)
- b. Convert  $127_{10}$  to
- i. BCD code (5 marks)
  - ii. Hexadecimal (5 marks)

### Question #4

- a. Derive a Boolean expression for the logic circuit shown in Fig. Q4 (6marks)

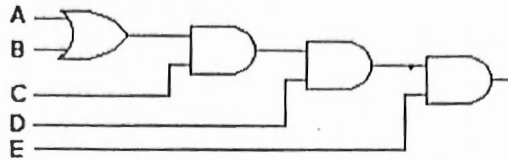


Fig Q4 for Question 4

- b. Given the truth table (Table Q4) below,
- Express X and Y in products of maxterms;
  - Obtain the simplified function in the sum of product form using Karnaugh map (14 marks)

Table Q4 Truth Table for Question 4

| A | B | C | X | Y |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

### Question #5

- a. Prove using any suitable method that;

$$f(A B C D) = ABCD + AB\bar{C}\bar{D} + ABC\bar{D} + AB\bar{C}D + ABCDE + AB\bar{C}\bar{D}\bar{E} + AB\bar{C}DE \text{ can be simplified to } AB. \quad (8 \text{ marks})$$

- b. A circuit that controls a given digital system has three inputs:  $x_1$ ,  $x_2$  and  $x_3$ . It has to recognise three different conditions:

- Condition A is true if  $x_3$  is true and either  $x_1$  is true or  $x_2$  is false
- Condition B is true if  $x_1$  is true and either  $x_2$  or  $x_3$  is false
- Condition C is true if  $x_2$  is true and either  $x_1$  is true or  $x_3$  is false

The control circuit must produce an output of 1 if at least two of the conditions A, B and C are true. Design the simplest circuit that can be used for this purpose. (12 marks)

### Question #6

- Design a 4-bit ring counter and explain briefly how the device can be used to control a sequence of operations. (7 marks)
- Why is a parallel counter faster than a ripple counter? (2 marks)
- What is multiplexing? Illustrate your answer using a neat diagram (4 marks)
  - Write out five applications of multiplexers (5 marks)
  - What is the difference between a decoder and demultiplexer? (2 marks)

**Question #7**

- a. A clocked JK flip flop is connected such that  $J=K=1$ . Draw the flip flop and its truth table.  
**(4 marks)**
- b. A ripple counter uses flip-flops having total propagation delay of 12 nano-seconds. If the counter is to be operated at 10MHz, how many flip-flops are required? What can be the highest MOD counter thus constructed?  
**(12 marks)**
- c. Using a neat sketch to show the distinction between a combinational circuit and a sequential circuit.  
**(4marks)**