



ELIZADE UNIVERSITY, ILARA-MOKIN, ONDO STATE
FACULTY OF ENGINEERING
DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

FIRST SEMESTER EXAMINATION, 2020/2021 ACADEMIC SESSION

COURSE TITLE: ELECTRIC CIRCUIT THEORY

COURSE CODE: EEE 317

EXAMINATION DATE: --RD MARCH, 2021

COURSE LECTURER: DR R. O. Alli-Oke

HOD's SIGNATURE

TIME ALLOWED: 3 HRS

INSTRUCTIONS:

1. ANSWER QUESTION 1 AND ANY OTHER FOUR QUESTIONS (TOTAL OF 5 QUESTIONS)
2. SEVERE PENALTIES APPLY FOR MISCONDUCT, CHEATING, POSSESSION OF UNAUTHORIZED MATERIALS DURING EXAM.
3. YOU ARE NOT ALLOWED TO BORROW CALCULATORS AND ANY OTHER WRITING MATERIALS DURING THE EXAMINATION.

QUESTION #1

- a) Consider the source-driven RC circuit shown in Figure 1a below. [10 marks]
- Find v_C for all times t .
 - Analytically determine the time constant. *Hint: this is the time at which $v_C(t) = 0.632v_C(0)$*

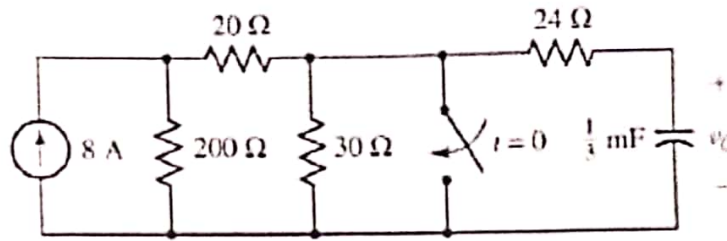


Figure 1a: Source-Driven RC Circuit

- b) The second-order filter in Figure 1b is used after the rectification stage of a power supply design. [10 marks]

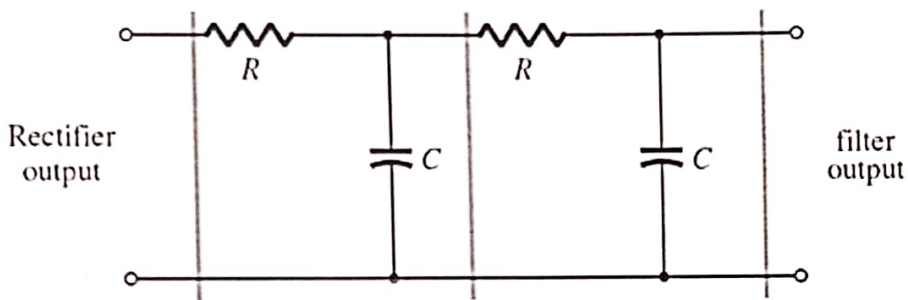


Figure 1b: Second-Order Low-Pass Filter

- With the aid of diagrams explain why a filter needed after rectification
- Let V_i and V_o represents phasors corresponding to input and output voltages respectively. Show that the transfer function $H(j\omega) = \frac{V_o}{V_i} = \frac{1}{(1-\omega^2 R^2 C^2) + 3j\omega RC}$. *Hint: Use the phasor-domain circuit*
- Analytically obtain the DC gain and AC gain from the expression obtained in (ii) above.
- Determine the -3 dB cut-off frequency f_c of this filter. *Hint set RC as τ , and solve for ω such that $|H(j\omega)| = \frac{1}{\sqrt{2}}$*
- Choose $R \geq 5 \text{ k}\Omega$ and C such that it has a DC gain of 0 dB and a bandwidth of 1 kHz.

QUESTION #2

- a) Consider the op-amp circuit shown in the Figure 2a below. Using only KCL, determine v_{out} . [4 marks]

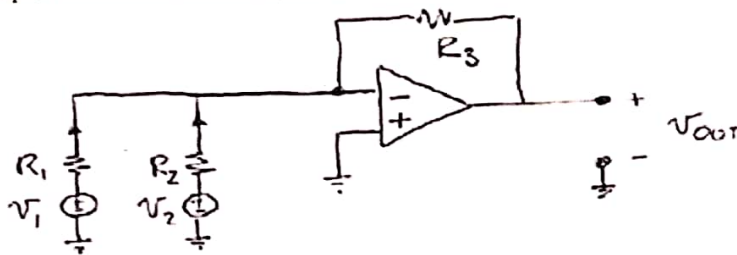


Figure 2a: Op-Amp Circuit

- b) Assume $v_o(0) = 5$ and use Laplace-domain analysis to determine $v_o(t)$. Hint: $\mathcal{L}\{e^{-t} u(t)\} = \frac{1}{s+1}$ and $\mathcal{L}\{\delta t\} = 1$.

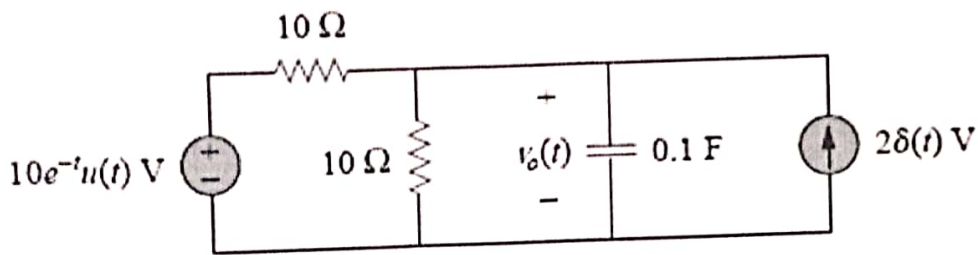


Figure 2b: Source-Driven RC Circuit

QUESTION #3

- a) Using phasor-domain analysis, determine the steady-state current $i(t)$ shown in Figure 3b. [4 marks]
- b) Use time-domain analysis to obtain the inductor current $i_L(t)$ for all times for the circuit in Figure 3a. [6 marks]

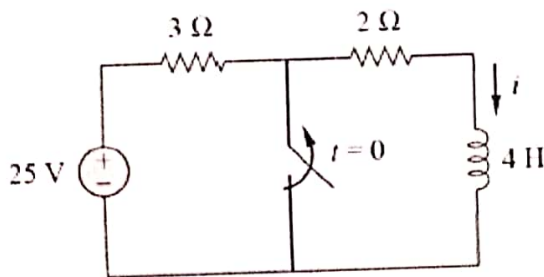


Figure 3a: R-L Network


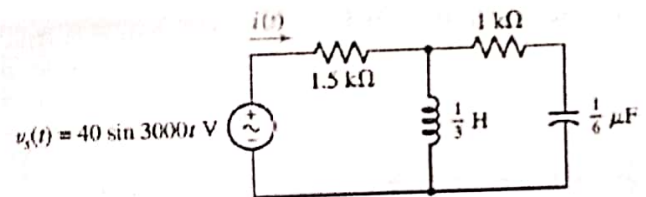


Figure 3b: A Sinusoidal-Excited Circuit

QUESTION #4

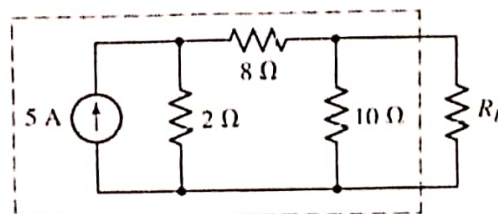- a) Using repeated source transformation, determine the Norton equivalent of network A. [4 marks]



Network A

Figure 5: Source Transformation

- b) Consider the schematic diagram of 2-bit op-amp-based R-2R ladder logic shown in Figure 4b. Use ONLY Thevenin's theorem to determine V_o . Do not use superposition theorem. [6 marks]

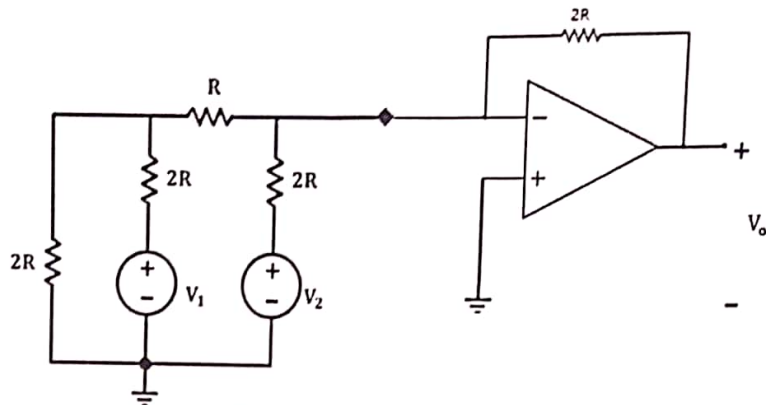


Figure 4b: Op-Amp Based R-2R ladder DAC Circuit

QUESTION #5

- a) Determine the current through the 10Ω resistor in Figure 1 using nodal analysis. [4 marks]

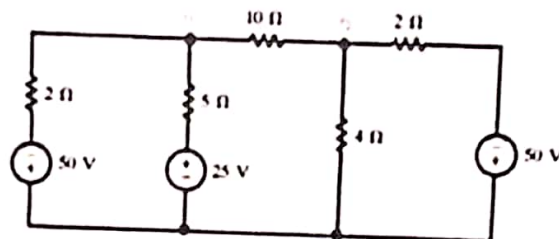


Figure 1: Resistive Circuit with Voltage Sources

- b) Let $V(s)$ be the Laplace-transform of $v(t)$ shown in Figure 5. Derive the expression for $V(s)$. [6 marks]

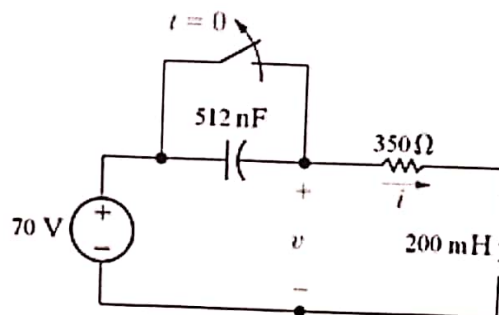


Figure 5: Source-Driven RLC Circuit

QUESTION #6

a) Compute the voltage v_o at the output port in Figure 3b, and the power absorbed by the voltage-dependent source.

[5 marks]

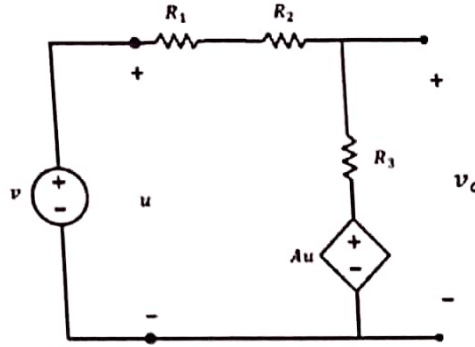


Figure 3b: Voltage-Dependent Source Circuit

b) Consider the single node-pair circuit below in in Figure 6b. We want to determine the current in the $3k\Omega$ resistor using Thevenin's theorem.

[5 marks]

- i. Find the Thevenin's network of network A.
- ii. Find the Thevenin's network of network B.
- iii. Draw the diagram of the reduced circuit diagram of Figure 6b by replacing network A & B with their respective Thevenin's network.
- iv. Use KVL to compute the current through the $3k\Omega$ resistor.

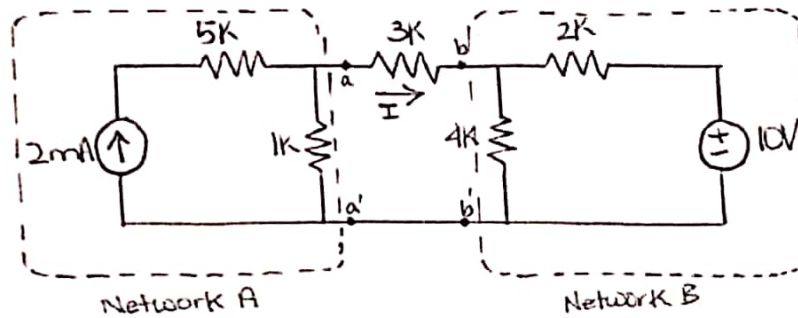


Figure 6b: Resistive Network

QUESTION #7

- a) Consider the network shown in Figure 7a. When $V = 10\text{ V}$ and $I = 0\text{ A}$, it is observed that $i = -1\text{ A}$ and $v = 5\text{ V}$. Additionally, when $I = 2\text{ A}$ and $V = 0$, it is observed that $v = 20\text{ V}$. With this information, determine R_1 , R_2 and R_3 . [4 marks]

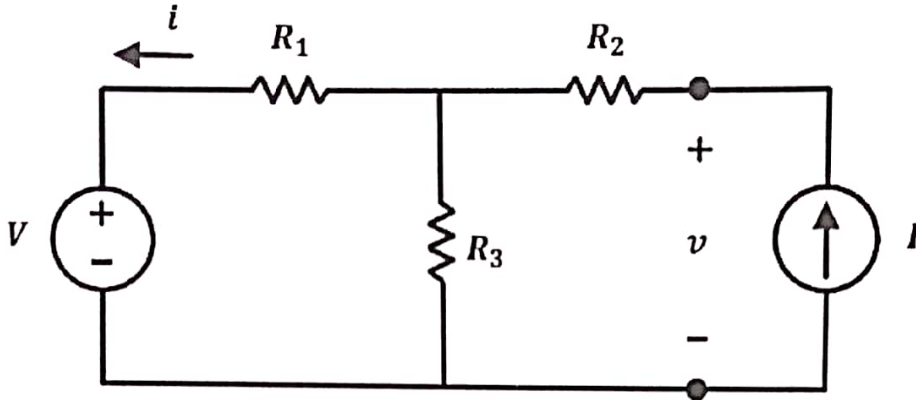


Figure 7a: Resistive Network

- b) Use phasor-domain analysis on the circuit shown in the figure (b) to determine the sinusoidal steady-state phasor currents I_1 , and I_2 [6 marks]

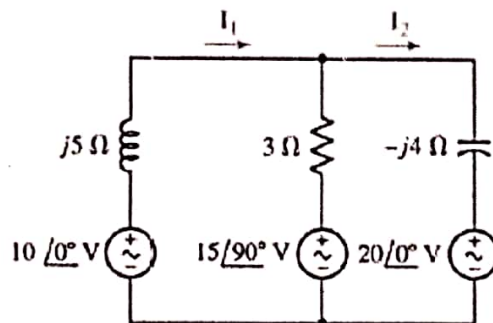


Figure 8: Phasor-Domain Analysis